

SINGLE CYCLE MIPS32 PROCESSOR

BY
YANDARAPU JAYA KUSHAL
GITHUB: [jayakushal24](#)

*This project was undertaken as a **personal learning initiative** to deepen my understanding of processor architecture, digital design, and the MIPS32 instruction set. The goal was to implement a functional **single-cycle processor** entirely in Verilog, simulating core components such as instruction decoding, register file handling, memory operations, and ALU computations.*

Through this project, I successfully developed a working MIPS32 processor capable of executing a variety of basic R-type and I-type instructions. The processor was verified using simulation waveforms and test programs written in hexadecimal format.

This hands-on experience significantly enhanced my practical knowledge of computer architecture, RTL design, and the functional flow of instruction execution in a CPU.

OVERVIEW

MIPS32 Overview

- 32 bit 32 general purpose Registers (GPRs), R0 to R31
- * R0 has Constant 0. Cannot write any other value to R0.
- A special purpose 32-bit program counter (PC)
- * points to next instruction in memory to be fetched & executed
- No flag registers (Zero, Carry, Sign flags etc).
- Very few addressing modes (register, immediate, register indexed, etc).
- * only load and store instructions can access memory.

MIPS32 Instruction Subset Being Considered:

1) Load and store →

LW R2, 12(R8) ↔ R2 = mem[R8 + 12]

SW R5, -10(R23) ↔ mem[R23 - 10] = R5

2) ALU →

ADD R1, R2, R3 ↔ R1 = R2 + R3

ADD R1, R2, R0 ↔ R1 = R2 + 0

SUB R12, R10, R8 ↔ R12 = R10 - R8

AND R20, R1, R5 ↔ R20 = R1 & R5

OR R11, R5, R6 ↔ R11 = R5 | R6

MUL R5, R6, R7 ↔ R5 = R6 * R7

Set less than → SLT R5, R11, R12 ↔ if R11 < R12, R5 = 1; else R5 = 0

* ALU (Immediate operand)

ADDI R1, R2, 25 ↔ R1 = R2 + 25

SUBI R5, R1, 150 ↔ R5 = R1 - 150

SLTI R2, R10, 10 ↔ if R10 < 10, R2 = 1, else R2 = 0

* Branch instructions

BEQZ R1, LOOP ↔ Branch to loop if R1 = 0

BNEQZ R5, LABEL ↔ Branch to label if R5 != 0

* Jump instructions

J loop ↔ Branch to loop unconditionally


* Halt execution

HLT


Classification

Three groups → R-type (register)
I-type (Immediate)
J-type (Jump)

(a) R-type

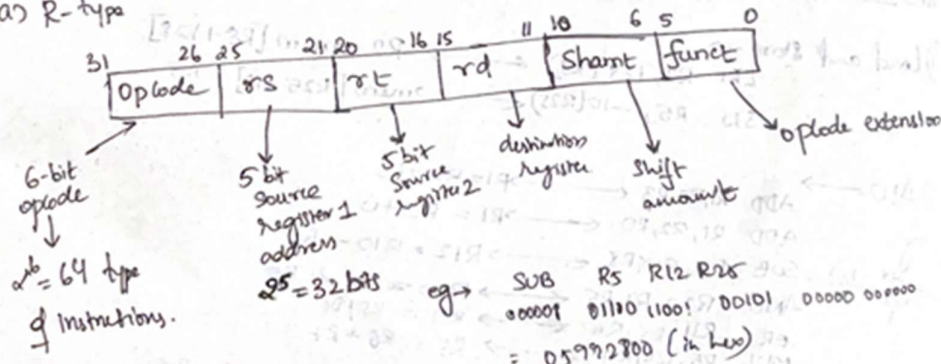


(b) I-type

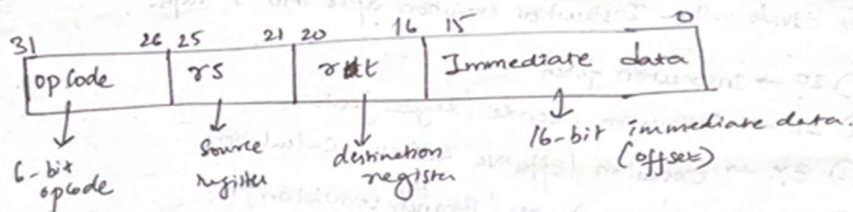

lw (load), sw (store), addi, subi, slti, bneqz, beqz.


(opcode can be chosen).

(c) J-type

 

*Only after decoding the instruction, we know if both registers rs & rt are reg. or just rs.
So, while decoding is going on, we can prefetch the registers in parallel.

MIPS32 ARCHITECTURE

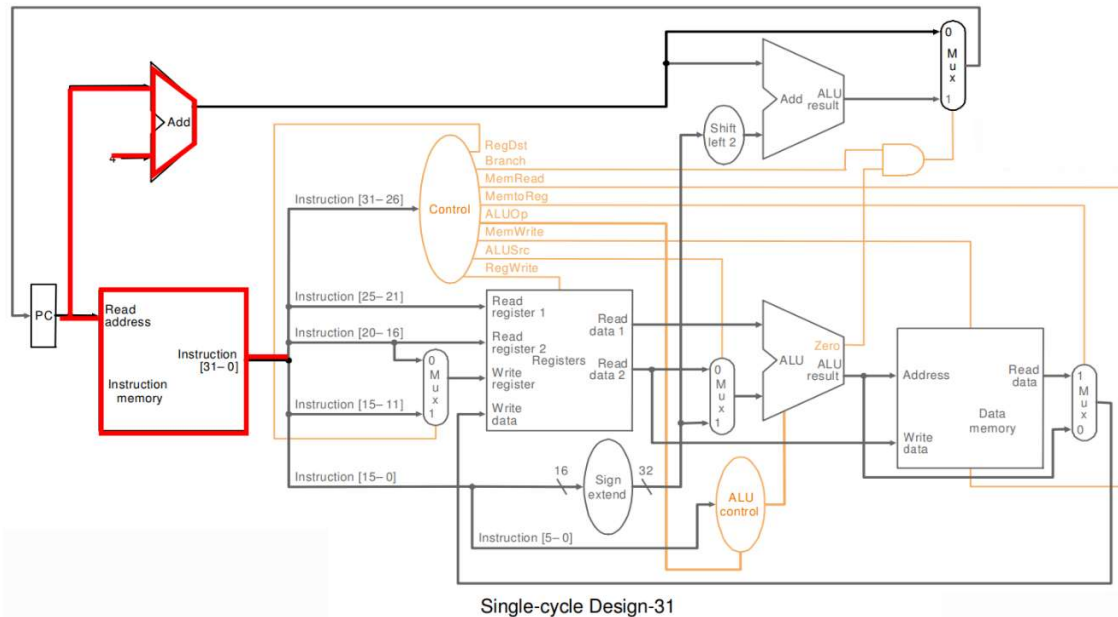

Source: <https://www.cs.nthu.edu.tw/~king/courses/cs4100/P51-proc.pdf>

NOTE: Code was written based on this architecture

ARCHITECTURE FUNCTION

1. Program Counter (PC)

- **Function:** Holds the address of the current instruction
- **Operation:** Updates every cycle to point to the next instruction address
- **Input:** New PC value (either $PC + 4$ or branch target)
- **Output:** Instruction memory read address

2. Instruction Memory

- **Function:** Stores all program instructions.
- **Operation:** Outputs the 32-bit instruction located at the address from the PC
- **Input:** 32-bit read address
- **Output:** 32-bit instruction

3. Instruction Fields

- **Function:** Breaks down the 32-bit instruction into individual fields for decoding and execution
- **Fields information:**
 - **Opcode (bits 31–26):** Specifies the instruction type (R-type, I-type, or J-type). This field determines the general operation category
 - **rs (bits 25–21):** Source register 1. This register supplies the first operand for the instruction
 - **rt (bits 20–16):** Source register 2 for R-type instructions or destination register for I-type instructions. For example, in an I-type load/store, this specifies the register involved
 - **rd (bits 15–11):** Destination register for R-type instructions. This is where the result of the computation is stored
 - **shamt (bits 10–6):** Shift amount field. Used **only** in shift instructions (like sll, srl, sra) to specify how many bits positions the bits in a register should be shifted. It is a 5-bit unsigned value allowing shifts from 0 to 31 bits
 - **funct (bits 5–0):** Function field. Used **only** in R-type instructions to specify the exact ALU operation to perform (such as add, subtract, AND, OR, set on less than, etc.). Since the opcode for all R-type instructions is the same, the funct field differentiates among various R-type operations

4. Control Unit

- **Function:** Generates control signals based on the opcode. //decides if the opcode is for R type /I type /Lw/ Sw
- **Operation:** Decides what each datapath element should do for the current instruction
- **Input:** Opcode (Instruction [31:26]).
- **Output:** Control signals:
 - RegDst, Branch, MemRead, MemtoReg, ALUOp, MemWrite, ALUSrc, RegWrite

5. Register memory

- **Function:** Stores all 32 general-purpose registers
- **Operation:**
 - Reads two source registers
 - Writes one destination register if RegWrite is enabled
- **Inputs:**
 - Read register 1, Read register 2
 - Write register, Write data, and RegWrite
- **Outputs:**
 - Read data 1, Read data 2

6. Sign-Extend module

- **Function:** Extends 16-bit immediate to 32-bit signed value
- **Input:** Instruction [15:0] (immediate)
- **Output:** 32-bit sign-extended immediate

7. ALU Control

- **Function:** Generates specific ALU operation code
- **Input:** ALUOp (from Control Unit) and function field (Instruction [5:0])
- **Output:** 4-bit control signal to ALU

8. ALU

- **Function:** Performs arithmetic and logic operations
- **Inputs:**
 - Operand A: Read data 1
 - Operand B: Either Read data 2 or sign-extended immediate (based on ALUSrc)
 - Control signal from ALU Control
- **Output:**
 - Result of the operation
 - Zero flag (used for branches)

9. Data Memory

- **Function:** Stores and retrieves data (for load/store instructions)
- **Inputs:**
 - Address (from ALU)
 - Write data (from register file)
 - Control: MemRead, MemWrite
- **Output:** Read data (used in load instructions)

10. MUX (Multiplexers)

- **MUX 1 (RegDst):** Chooses between rt and rd as destination register
- **MUX 2 (ALUSrc):** Chooses second ALU operand between Read data 2 and sign-extended immediate
- **MUX 3 (MemtoReg):** Chooses between ALU result and Data Memory output for writing back to register
- **MUX 4 (PCSrc):** Chooses next PC value: PC + 4 or branch address

11. Shift Left 2

- **Function:** Shifts the sign-extended immediate left by 2 bits ($\times 4$), used for branch address calculation
- **Input:** Sign-extended immediate
- **Output:** Shifted value to be added to PC + 4

12. Adder (PC + 4 and Branch Target)

- **Adder 1:** Computes PC + 4.
- **Adder 2:** Computes branch target address (PC + 4 + shifted immediate).

13. Branch Logic

- **Function:** Determines if a branch should be taken.
- **Inputs:**
 - Zero flag from ALU.
 - Branch control signal.
- **Output:** Enables MUX 4 to select branch address if condition is met.

CODE:

PC Block

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sources_1/new/program_counter.v

```
1  `timescale 1ns / 1ps
2
3  module program_counter(
4      input clk,
5      input reset,
6      input [31:0]pc,
7      output reg [31:0]next_pc
8  );
9      always @(posedge clk or posedge reset) begin
10         if (reset)
11             next_pc<=32'b0;
12         else
13             next_pc<=pc;//pc is not directly incremented..as there might be branch and jump instructions
14         end
15     endmodule
```

PC adder Block

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sources_1/new/pc_add.v

```
1  `timescale 1ns / 1ps
2
3
4  module pc_add(
5      input [31:0]pc_in,
6      output [31:0]pc_out
7  );
8      assign pc_out = pc_in+4;
9  endmodule
10
```

MUX block

D:\vivado_projects\Project_M32\MIPS32\MIPS32.srcs/sources_1/new/mux2x1.v

```
1 timescale 1ns / 1ps
2
3 //used between registers memory(after) and ALU(before)
4
5 //used between data memory (after) and registers memory(before)
6
7 module mux2x1 (
8     input [31:0]in1,
9     input [31:0]in0,
10    input sel,
11    output [31:0]out
12);
13
14    assign out= sel? in1:in0;
15
16 endmodule
17
18
19 //used between instruction memroy(after) and register memory(before)
20 module mux2x1_5b(
21     input [4:0]in1,
22     input [4:0]in0,
23     input sel,
24     output [4:0]out
25 );
26
27    assign out= sel? in1:in0;
28
29 endmodule
30
```

Instruction memory Block

D:\vivado_projects\Project_M32\MIPS32\MIPS32.srcs/sources_1/new/instruction_memory.v

```
1 timescale 1ns / 1ps
2
3 module instruction_memory(
4     input clk, reset,
5     input [31:0]read_address,
6     output reg [31:0]instruction
7 );
8
9     reg [31:0]mem[63:0];
10    integer i;
11
12    initial begin
13        for (i=0; i<64; i=i+1)
14            mem[i] = 32'h00000000;
15
16        mem[0] = 32'h20080005; // addi $t0, $zero, 4
17        mem[1] = 32'h20090003; // addi $t1, $zero, 3
18        mem[2] = 32'h01095020; // add $t2, $t0, $t1
19        mem[3] = 32'h012A5822; // sub $t3, $t1, $t2
20        mem[4] = 32'hAC0A0004; // sv $t2, 4($zero)
21        mem[5] = 32'h8C0C0004; // lw $t4, 4($zero)
22        mem[6] = 32'h110C0002; // beq $t0, $t4, label (2 offset)///branching inst branch=1 zero =0..next inst not skipped
23        mem[7] = 32'h200D0001; // addi $t5, $zero, 1
24        mem[8] = 32'h200D0002; // addi $t5, $zero, 2
25        mem[9] = 32'h11AD0001; // beq $t5, $t5, label (1 offset)///branching branch=1 and zero=1
26        mem[10] = 32'h200E00FF; // addi $t6, $zero, 255//////////Skipped Instruction
27        mem[11] = 32'h200E0001; // addi $t6, $zero, 1
28        mem[12] = 32'h200E0002; // addi $t6, $zero, 2
29        mem[13] = 32'h200E0003; // addi $t6, $zero, 3
30    end
31
32    always @(*) begin
33        instruction=mem[read_address>>2]; //might have to divide by 4 here...depending onn value initialization
34    end
35
36 endmodule
37
```


Register memory Block

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srscs/sources_1/new/registerts.v

```
1  `timescale 1ns / 1ps
2
3
4  module registerts(
5      input clk,
6      input [31:0]write_data,
7      input [4:0]write_register,read_register1,read_register2,
8      input reg_write,
9      output [31:0]read_data1,read_data2
10 );
11
12     reg [31:0] register_mem[31:0];
13
14     integer i;
15     initial begin
16         for (i=0; i<32; i=i+1)
17             register_mem[i] = 32'd0;
18     end
19     always @(posedge clk)begin
20
21         if (reg_write && write_register!=0)begin //1st register is 0(fixed in MIPS)
22             register_mem[write_register]=write_data;
23         end
24     end
25     assign read_data1=register_mem[read_register1];
26     assign read_data2=register_mem[read_register2];
27
28
29 endmodule
30
```

Sign extend block

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srscs/sources_1/new/sign_extend.v

```
1  `timescale 1ns / 1ps
2
3
4  module sign_extend(
5      input [15:0]in,
6      output [31:0]out
7  );
8
9      assign out =({16{in[15]}},in);
10 endmodule
11
```

CONTROL BLOCK

D:/Vivado_projects/M32/MIPS32/MIPS32.srcs/sources_1/new/control.v

```
1 timescale 1ns / 1ps
2
3 module control(
4     input [5:0]opcode,
5     output reg RegWrite,
6     output reg MemRead,
7     output reg MemWrite,
8     output reg MemToReg,
9     output reg ALUSrc,
10    output reg Branch,
11    output reg RegDst,
12    output reg [1:0] ALUOp
13);
14
15    always @(*) begin
16        case (opcode)
17            6'b000000: //R type
18                begin
19                    RegDst= 1'b1;ALUSrc= 1'b0;MemToReg= 1'b0;RegWrite= 1'b1;
20                    MemRead= 1'b0;MemWrite= 1'b0;Branch= 1'b0;ALUOp= 2'b10;
21                end
22
23            6'b100011: // lw
24                begin
25                    RegDst= 1'b0;ALUSrc= 1'b1;MemToReg= 1'b1;RegWrite= 1'b1;
26                    MemRead= 1'b1;MemWrite= 1'b0;Branch= 1'b0;ALUOp= 2'b00;
27                end
28
29            6'b101011: // sv
30                begin
31                    RegDst= 1'bx;ALUSrc= 1'b1;MemToReg= 1'bx;RegWrite= 1'b0;
32                    MemRead= 1'b0;MemWrite= 1'b1;Branch= 1'b0;ALUOp= 2'b00; // ALU performs add to cal address
33                end
34
35            6'b000100: // beq
36                begin
37                    RegDst= 1'bx;ALUSrc= 1'b0;MemToReg= 1'bx;RegWrite= 1'b0;
38                    MemRead= 1'b0;MemWrite= 1'b0;Branch= 1'b1;ALUOp= 2'b01;
39                end
40
41            6'b001000: // addi (I-type ALU immediate)
42                begin
43                    RegDst= 1'b0;ALUSrc= 1'b1;MemToReg= 1'b0;RegWrite= 1'b1;
44                    MemRead= 1'b0;MemWrite= 1'b0;Branch= 1'b0;ALUOp= 2'b00; //ADD
45                end
46
47            default:
48                begin
49                    RegDst= 1'b0;ALUSrc= 1'b0;MemToReg= 1'b0;RegWrite= 1'b0;
50                    MemRead= 1'b0;MemWrite= 1'b0;Branch= 1'b0;ALUOp= 2'b00;
51                end
52            endcase
53        end
54
55
56
57 endmodule
58
```

ALU CONTROL BLOCK

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sources_1/new/ALU_control.v

```
1 `timescale 1ns / 1ps
2
3 module ALUControl(
4     input [1:0] ALUOp,          //output from Control
5     input [5:0] funct,          //from instruction[5:0] for r type
6     output reg [3:0] operation
7 );
8
9     always @(*) begin
10         case (ALUOp)
11             2'b00: operation = 4'b0000; //lw,sw,addi..add
12             2'b01: operation = 4'b0001; //beq => SUBTRACT
13
14             2'b10: begin //for r type ...decode funct field
15                 case (funct)
16                     6'b100000: operation = 4'b0000; //add
17                     6'b100010: operation = 4'b0001; //sub
18                     6'b100100: operation = 4'b0010; //and
19                     6'b100101: operation = 4'b0011; //or
20                     6'b101010: operation = 4'b0111; //slt
21                     6'b100110: operation = 4'b0100; //xor
22                     6'b000000: operation = 4'b0101; //Shift left logical
23                     6'b000010: operation = 4'b0110; //Shift right logical
24                     default: operation = 4'b0000;
25                 endcase
26             end
27
28             default: operation = 4'b0000;
29         endcase
30     end
31
32 endmodule
```

ALU BLOCK

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sources_1/new/ALU.v

```
1 `timescale 1ns / 1ps
2
3 module ALU(
4     input [31:0] A,
5     input [31:0] B,
6     input [3:0] operation,
7     output reg [31:0] Result,
8     output reg Zero
9 );
10
11     always @(A or B or operation) begin
12         case (operation)
13             4'b0000: Result = A + B;
14             4'b0001: Result = A - B;
15             4'b0010: Result = A & B; //and
16             4'b0011: Result = A | B; //or
17             4'b0100: Result = A ^ B; //xor
18             4'b0101: Result = B << A[4:0]; //logical shift left
19             4'b0110: Result = B >> A[4:0]; //logical shift right
20             4'b0111: Result = (A < B) ? 32'd1 : 32'd0;
21             default: Result = 32'b0;
22         endcase
23
24         Zero = (Result == 32'b0) ? 1 : 0; //to be used for branching op
25     end
26
27 endmodule
28
```

Data Memory BLOCK

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sources_1/new/data_memory.v

```
1  `timescale 1ns / 1ps
2
3
4  module data_memory(
5      input clk,
6      input rst,
7      input MemRead,
8      input MemWrite,
9      input [31:0]address,
10     input [31:0]write_data,
11     output[31:0]read_data
12 );
13     reg [31:0]data_memory[31:0];
14
15     integer i;
16     assign read_data=(MemRead)? data_memory[address>>2]:32'b00;
17
18
19     always @(posedge clk or posedge rst) begin
20         if (rst ) begin
21             for (i=0; i<32; i=i+1) begin
22                 data_memory[i] = 32'b00;
23             end
24         end else if (MemWrite) begin
25             data_memory[address>>2]=write_data;
26         end
27     end
28
29 endmodule
30
```

Adder Branch Block

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sources_1/new/adder_branch.v

```
1  `timescale 1ns / 1ps
2
3
4  module adder_branch(
5      input [31:0]pc,
6      input [31:0]branch_jump,
7      output [31:0]destination
8  );
9
10     assign destination = pc+ branch_jump;
11
12 endmodule
```

TOP MODULE

D:/Vivado_projects/M32/MIPS32/MIPS32.srcs/sources_1/new/MIPS32_TOP.v

```
1  `timescale 1ns / 1ps
2
3  module MIPS32_TOP(
4      input clk,
5      input rst
6  );
7
8      // Wires
9      wire [31:0] pc_wire, pc_out_wire, pc_next_wire, decode_wire, read_data1, read_data2, reg_mux_alu_out, sign_extension_out, ALU_result, read_data, write_data, Adder_result;
10     wire [4:0] write_reg_mux;
11     wire [1:0] ALUOp;
12     wire [3:0] operation;
13     wire RegDst, RegWrite, ALUSrc, MemRead, MemWrite, MemToReg, Branch, Zero;
14
15     // Program Counter
16     program_counter PC(
17         .clk(clk), .reset(rst), .pc(pc_wire), .next_pc(pc_out_wire)
18     );
19
20     // PC Adder
21     pc_add PC_Adder(
22         .pc_in(pc_out_wire), .pc_out(pc_next_wire)
23     );
24
25     // PC mux
26     mux2x1 pc_mux(
27         .in0(pc_next_wire), .in1(Adder_result), .sel(Branch & Zero), .out(pc_wire)
28     );
29
30     // instruction memory
31     instruction_memory Instr_Mem(
32         .reset(rst), .clk(clk), .read_address(pc_out_wire), .instruction(decode_wire)
33     );
34
35     // Write register mux
36     mux2x1_5b wr_reg_mux(
37         .in0(decode_wire[20:16]), .in1(decode_wire[15:11]), .sel(RegDst), .out(write_reg_mux)
38     );
39
40     // Register memory
41     registers Reg_mem(
42         .clk(clk), .reg_write(RegWrite), .write_data(write_data), .write_register(write_reg_mux), .read_register1(decode_wire[25:21]),
43         .read_register2(decode_wire[20:16]), .read_data1(read_data1), .read_data2(read_data2)
44     );
45
46     // Sign extend
47     sign_extend sign_ext(
48         .in(decode_wire[15:0]), .out(sign_extension_out)
49     );
50
51     // ALU input mux
52     mux2x1 reg_mux_alu(
53         .in0(read_data2), .in1(sign_extension_out), .sel(ALUSrc), .out(reg_mux_alu_out)
54     );
55
56     // Control unit
57     control control(
58         .opcode(decode_wire[31:26]), .RegWrite(RegWrite), .MemRead(MemRead), .MemWrite(MemWrite),
59         .MemToReg(MemToReg), .ALUSrc(ALUSrc), .Branch(Branch), .RegDst(RegDst), .ALUOp(ALUOp)
60     );
61
62     // ALU control
63     ALUControl alu_control(
64         .funct(decode_wire[5:0]), .ALUOp(ALUOp), .operation(operation)
65     );
66
67     // ALU
68     ALU alu_block(
69         .A(read_data1), .B(reg_mux_alu_out), .operation(operation), .Result(ALU_result), .Zero(Zero)
70     );
71
72     // data memory
73     data_memory dat_mem(
74         .clk(clk), .rst(rst), .MemRead(MemRead), .MemWrite(MemWrite), .address(ALU_result),
75         .write_data(read_data2), .read_data(read_data)
76     );
77
78     // Mem to Reg Mux
79     mux2x1 datmem_mux_regmem(
80         .in0(ALU_result), .in1(read_data),
81         .sel(MemToReg), .out(write_data)
82     );
83
84     // branch address adder
85     adder_branch adder(
86         .pc(pc_next_wire), .branch_jump(sign_extension_out << 2), .destination(Adder_result)
87     );
88
89     endmodule
90
```

VERIFICATION

TESTBENCH

D:/Vivado_projects/Project_M32/MIPS32/MIPS32.srcs/sim_1/new/MIPS32_tb.v

```
1  `timescale 1ns / 1ps
2
3
4  module MIPS32_tb();
5
6      reg clk, rst;
7      MIPS32_TOP DUT (.clk(clk), .rst(rst));
8
9      initial begin
10         clk = 0;
11     end
12     always #25 clk = ~clk; //clk gen
13
14     initial begin
15         rst = 1'b1;
16         #50;
17         rst = 1'b0;
18         #2000;
19         $finish;
20     end
21
22 endmodule
```

TABULATION:

PC (HEX)	INSTRUCTION	OPERATION DESCRIPTION	RESULT/VALUE STORED
0X00	addi \$t0, \$zero, 4	Load 4 into \$t0	\$t0 = 4
0X04	addi \$t1, \$zero, 3	Load 3 into \$t1	\$t1 = 3
0X08	add \$t2, \$t0, \$t1	Add \$t0 + \$t1 → \$t2	\$t2 = 4 + 3 = 7
0X0C	sub \$t3, \$t1, \$t2	Subtract \$t1 - \$t2 → \$t3	\$t3 = 3 - 7 = -4 (2's complement)
0X10	sw \$t2, 4(\$zero)	Store \$t2 to memory address 4	mem[4] = 7
0X14	lw \$t4, 4(\$zero)	Load value from memory address 4 into \$t4	\$t4 = 7
0X18	beq \$t0, \$t4, 2	Branch if \$t0 == \$t4 → Not taken	No branch, continue
0X1C	addi \$t5, \$zero, 1	Load 1 into \$t5	\$t5 = 1
0X20	addi \$t5, \$zero, 2	Load 2 into \$t5 (overwrites previous value)	\$t5 = 2
0X24	beq \$t5, \$t5, 1	Branch taken (since \$t5 == \$t5)	PC → 0x2C
0X28	addi \$t6, \$zero, 255	Skipped due to branch from 0x24	—
0X2C	addi \$t6, \$zero, 1	Load 1 into \$t6	\$t6 = 1
0X30	addi \$t6, \$zero, 2	Load 2 into \$t6	\$t6 = 2
0X34	addi \$t6, \$zero, 3	Load 3 into \$t6	\$t6 = 3

Instruction Explanation:

Instruction @ 0x00 Assembly: addi \$t0, \$zero, 5
Hex: 20080005
Binary: 001000 00000 01000 0000 0000 0000 0101
Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01000 → \$t0
- immediate: 0000 0000 0000 0101 → 5

Instruction @ 0x04 Assembly: addi \$t1, \$zero, 3
Hex: 20090003
Binary: 001000 00000 01001 0000 0000 0000 0011
Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01001 → \$t1
- immediate: 0000 0000 0000 0011 → 3

Instruction @ 0x08 Assembly: add \$t2, \$t0, \$t1
Hex: 01095020
Binary: 000000 01000 01001 01010 00000 100000
Type: R-type

- opcode: 000000
- rs: 01000 → \$t0
- rt: 01001 → \$t1
- rd: 01010 → \$t2
- shamt: 00000
- funct: 100000 → add

Instruction @ 0x0C Assembly: sub \$t3, \$t1, \$t2
Hex: 012A5822
Binary: 000000 01001 01010 01011 00000 100010
Type: R-type

- opcode: 000000
- rs: 01001 → \$t1
- rt: 01010 → \$t2
- rd: 01011 → \$t3

- shamt: 00000
- funct: 100010 → sub

Instruction @ 0x10 Assembly: sw \$t2, 4(\$zero)
 Hex: AC0A0004
 Binary: 101011 00000 01010 0000 0000 0000 0100
 Type: I-type

- opcode: 101011 → sw
- rs: 00000 → \$zero
- rt: 01010 → \$t2
- immediate: 0000 0000 0000 0100 → 4

Instruction @ 0x14 Assembly: lw \$t4, 4(\$zero)
 Hex: 8C0C0004
 Binary: 100011 00000 01100 0000 0000 0000 0100
 Type: I-type

- opcode: 100011 → lw
- rs: 00000 → \$zero
- rt: 01100 → \$t4
- immediate: 0000 0000 0000 0100 → 4

Instruction @ 0x18 Assembly: beq \$t0, \$t4, 2
 Hex: 110C0002
 Binary: 000100 01000 01100 0000 0000 0000 0010
 Type: I-type

- opcode: 000100 → beq
- rs: 01000 → \$t0
- rt: 01100 → \$t4
- immediate: 0000 0000 0000 0010 → 2

Instruction @ 0x1C Assembly: addi \$t5, \$zero, 1
 Hex: 200D0001
 Binary: 001000 00000 01101 0000 0000 0000 0001
 Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01101 → \$t5
- immediate: 0000 0000 0000 0001 → 1

Instruction @ 0x20 Assembly: addi \$t5, \$zero, 2
 Hex: 200D0002
 Binary: 001000 00000 01101 0000 0000 0000 0010
 Type: I-type

- opcode: 001000 → addi

- rs: 00000 → \$zero
- rt: 01101 → \$t5
- immediate: 0000 0000 0000 0010 → 2

Instruction @ 0x24 Assembly: beq \$t5, \$t5, 1
 Hex: 11AD0001
 Binary: 000100 01101 01101 0000 0000 0000 0001
 Type: I-type

- opcode: 000100 → beq
- rs: 01101 → \$t5
- rt: 01101 → \$t5
- immediate: 0000 0000 0000 0001 → 1

Instruction @ 0x28 Assembly: addi \$t6, \$zero, 255
 Hex: 200E00FF
 Binary: 001000 00000 01110 0000 0000 1111 1111
 Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01110 → \$t6
- immediate: 0000 0000 1111 1111 → 255

(Skipped if branch taken)

Instruction @ 0x2C Assembly: addi \$t6, \$zero, 1
 Hex: 200E0001
 Binary: 001000 00000 01110 0000 0000 0000 0001
 Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01110 → \$t6
- immediate: 0000 0000 0000 0001 → 1


Instruction @ 0x30 Assembly: addi \$t6, \$zero, 2
 Hex: 200E0002
 Binary: 001000 00000 01110 0000 0000 0000 0010
 Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01110 → \$t6
- immediate: 0000 0000 0000 0010 → 2

Instruction @ 0x34 Assembly: addi \$t6, \$zero, 3
 Hex: 200E0003
 Binary: 001000 00000 01110 0000 0000 0000 0011
 Type: I-type

- opcode: 001000 → addi
- rs: 00000 → \$zero
- rt: 01110 → \$t6
- immediate: 0000 0000 0000 0011 → 3

Waveform:

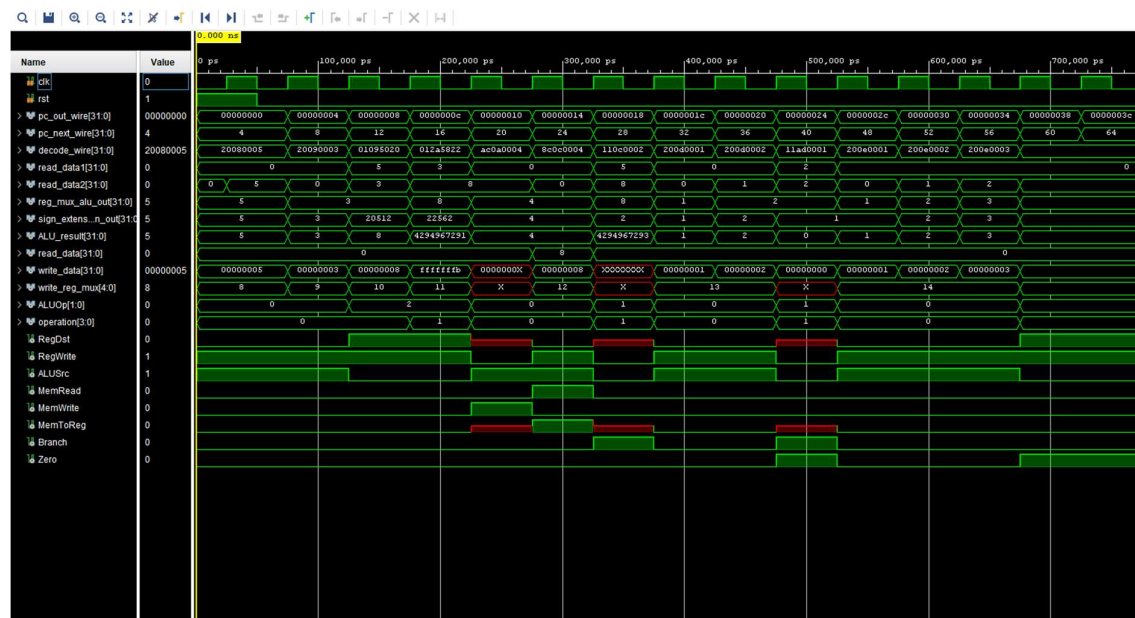

Result:

Single Cycle MIPS32 ISA Processor for my custom instruction (R type, I type, LW, SW) is **Successfully built**. The design is **verified**.

FUTURE WORK:

Need to modify the code so that it supports Jump instructions.

Idea to Implement:

1. Add a Jump reg to the control block to Identify opcode (6'b000010) and set it to 1.
2. Create a module for this:
jump address = {PC+4[31:28], decode_wire [25:0], 2'b00};
3. In1 of mux is jump address and in0 is (pc+4) pc adder. And select line is jump wire.
4. The output of this mux is connected to in0 of mux.

the best place to insert the Jump MUX is just before the top-right MUX.

Theory for JUMP Instruction Execution:

1. Why Shift Left by 2?

MIPS instructions are **word-aligned** — each instruction starts at an address divisible by 4 (e.g., 0x00000000, 0x00000004, 0x00000008, etc.).

So the actual memory address of any instruction will **always end in 00 in binary**.

2. Why Take PC+4[31:28]?

This is because MIPS jump instructions **only jump within the current 256MB memory block**.

Each 256MB block has the same top 4 bits in a 32-bit address:

- e.g., 0x00400000 to 0x004FFFFF all have top 4 bits as 0x0.

So, we just copy those bits from the current PC + 4.

Jump stays within the same region of the memory, which is how MIPS J-type instructions are defined.

Term	Value	Why?
instruction [25:0]	26 bits	Jump instruction field
After shift <<2	28 bits	Word to byte address
Top 4 bits from PC+4[31:28]	4 bits	To complete full 32-bit address
Max jumpable range	256 MB	Because $2^{28} = 256 \text{ MB}$

3. The offset is 26 bit. It specifies what address it should jump to. If you modify it by left shift twice. Will it change the address?

No, it doesn't "change" the address. In fact, **left-shifting by 2 is necessary**, because the 26-bit value is **not a byte address**, but a **word address**.

Example:

If the jump target is **instruction 100**, it lives at **address $100 \times 4 = 400$ bytes**.

Addressing is based on Bytes.. it should jump to 400th location.

the 26-bit field in the instruction is Word address

But the actual memory address is $\text{Word Address} \times 4 \rightarrow$ which means shift left by 2 bits

Example:

instruction [25:0] = 26'b000000_000000_000000_000000_000100 (decimal 4)

It refers to **instruction number 4**, located at byte address = $4 \times 4 = 16 = 0x10$

4.256 MB region concept?? why the restriction for jumpable range?

The upper 4 bits PC+4[31:28] define which **256 MB "region"** you're in.

That is:

- 0x0--- ---- to 0x0FFF FFFF \rightarrow First 256 MB
-
- 0xF--- ---- to 0xFFFF FFFF \rightarrow Last 256 MB

So, when jumping, you're **stuck in the same 256 MB region** as where you came from. The top 4 bits from PC+4 are **not changeable** by the jump instruction.

Restriction: this goes into **ISA design trade-offs** and hardware simplicity.

A jump (j) instruction format: | opcode (6) | target address (26) |

That leaves only **26 bits** for the target address.

Byte Addressing + Word Alignment: 26 bits + shift by 2 = 28 bits = 256 MB range

jump address = {PC+4[31:28], instruction [25:0], 2'b00};

This means:

- Jump can only **replace the lower 28 bits** of PC.
- **Top 4 bits stay the same**, so the jump stays **within the current 256 MB segment**.

REFERENCES:

ARCHITECTURE DESIGN:

<https://www.cs.nthu.edu.tw/~king/courses/cs4100/P51-proc.pdf>

<https://courses.cs.washington.edu/courses/cse378/09wi/lectures/lec07.pdf>

<https://docslib.org/download/952472/mips32-architecture-for-programmers-volume-i-introduction-to-the-mips32-architecture>

<https://cs.stanford.edu/people/eroberts/courses/soco/projects/risc/mips/index.html>